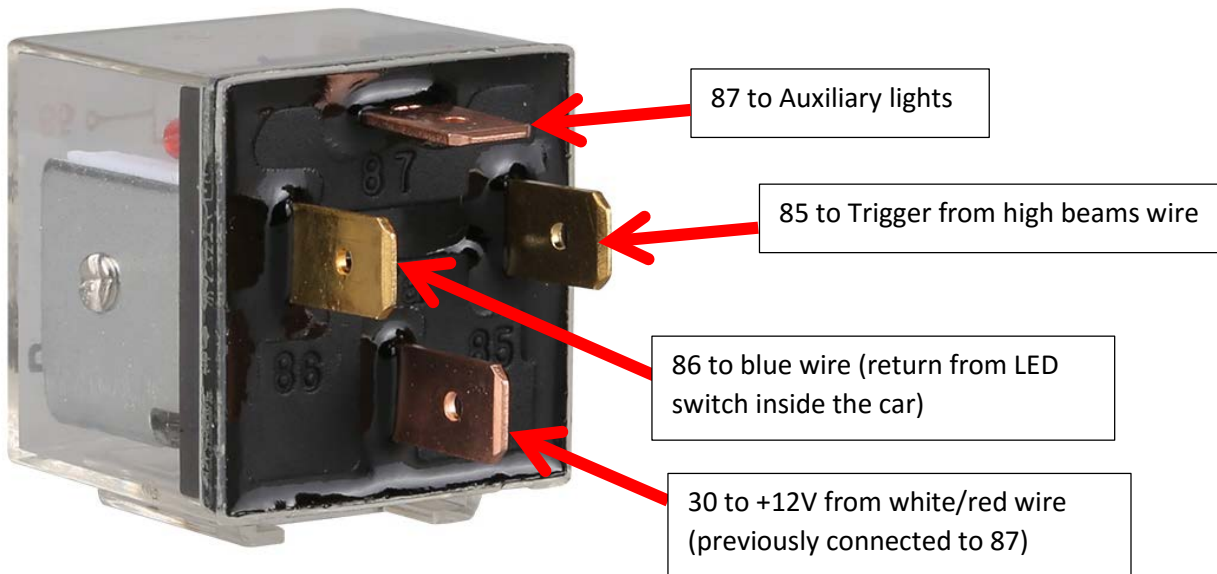
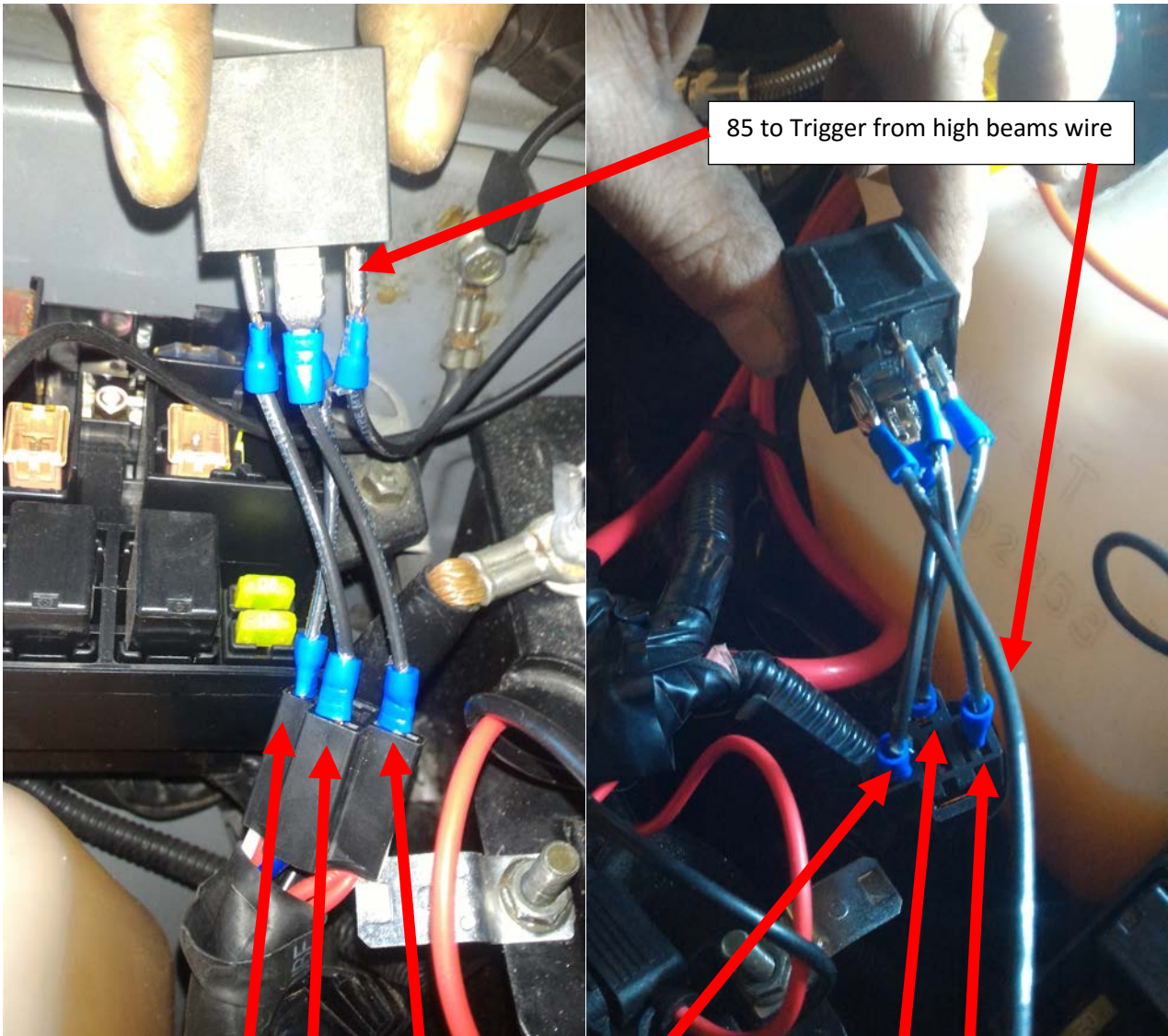


1. Tap the white wire from the high beam connector. It should be 12V when off and 0V when on. This is a negative trigger.



2. Pull the relay off the connector and pull back the wrap at the back of the connectors to see the wires and their colors. The back of the relay has 4 pins identified with the following numbers 30, 85, 86 and 87.
3. Wire as indicated below





85 to Trigger from high beams wire

87 to Auxiliary lights

86 to blue wire (return from LED switch inside the car)

30 to +12V from white/red wire (previously connected to 87)

4. Use shrink wrap to isolate all the wires and secure them in place. Use additional electrical tape as needed.